

# EE2703 : Applied Programming Lab

## Assignment 8

Potta Muni Asheesh  
EE19B048

May 23, 2021

### 1 Introduction

In this assignment, circuit analysis using Laplace transforms is done using `sympy` as a tool for symbolic algebra.

### 2 Low pass filter

The following low pass filter is considered.

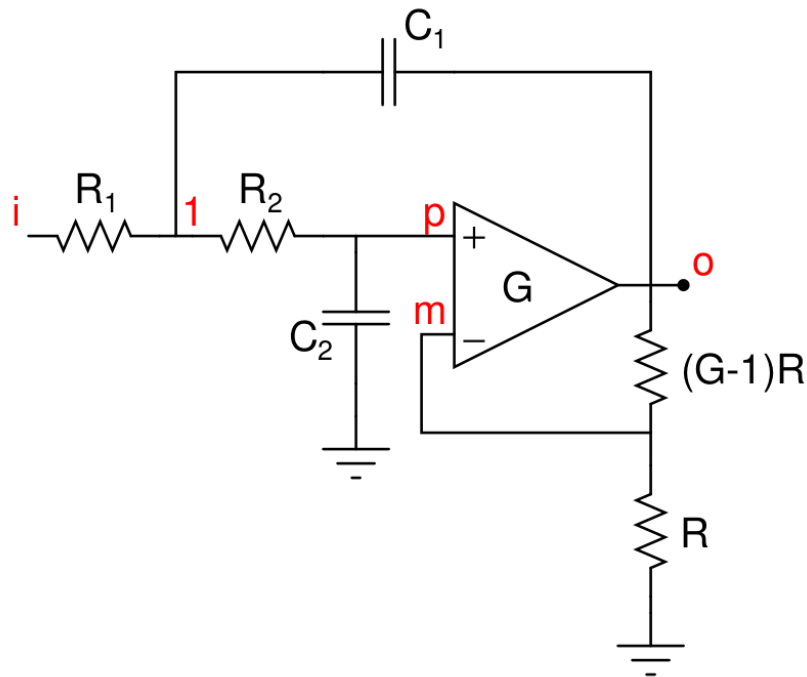


Figure 1: Circuit diagram of lowpass filter

where, the Op-Amp is ideal and  $G = 1.586$ ,  $R_1 = R_2 = 10k\Omega$  and  $C_1 = C_2 = 10pF$ . This gives a second order Butter-worth filter with cutoff frequency of  $10/2\pi$  MHz. As the

op-amp is considered ideal, the circuit equations are

$$V_m = \frac{V_o}{G} \quad (1)$$

$$V_p = \frac{V_1}{1 + sC_2R_2} \quad (2)$$

$$V_p = V_m \quad (3)$$

$$\frac{V_i - V_1}{R_1} + \frac{V_p - V_1}{R_2} + sC_1(V_o - V_i) = 0 \quad (4)$$

These equations upon solving give the  $V_i$  to  $V_o$  transfer function as

$$\frac{V_o}{V_i} = \frac{1.586}{1 + \frac{1.414s}{10^7} + \frac{s^2}{10^{14}}}$$

This circuit analysis is done in python using sympy module.

The four circuit equations are solved by rewriting them as a matrix equation and using sympy to solve the matrix equation.

$$\begin{pmatrix} 0 & 0 & 1 & \frac{-1}{G} \\ \frac{1}{1+sR_2C_2} & -1 & 0 & 0 \\ 0 & 1 & -1 & 0 \\ \frac{1}{R_1} + \frac{1}{R_2} + sC_1 & \frac{-1}{R_2} & 0 & -sC_1 \end{pmatrix} \begin{pmatrix} V_1 \\ V_p \\ V_m \\ V_o \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ \frac{V_i(s)}{R_1} \end{pmatrix}$$

A function is defined in python takes, the circuit parameters and Laplace transform of input signal, as arguments and returns the matrix as A, the input vector as b and the voltage vector as V.

```
import numpy as np
import matplotlib.pyplot as plt
import scipy.signal as sp
import sympy as sym

def lowpass(R1,R2,C1,C2,G,Vi):
    s = sym.symbols('s')
    A = sym.Matrix([[0,0,1,-1/G],[1/(1 + s*C2*R2),-1,0,0],[0,1,-1,0],[1/
    ↪ R1+1/R2+s*C1,-1/R2, 0, -s*C1]])
    b = sym.Matrix([0,0,0,Vi/R1])
    V = A.inv()*b
    return (A, b, V)
```

The Frequency response of the low pass filter as obtained by extracting the coefficients of the numerator and the denominator of the rational expression for  $V_o$  in the array V. This is done as shown below. The frequency response obtained is shown below. The DC gain of the filter is  $20\log(G) = 4dB$ .

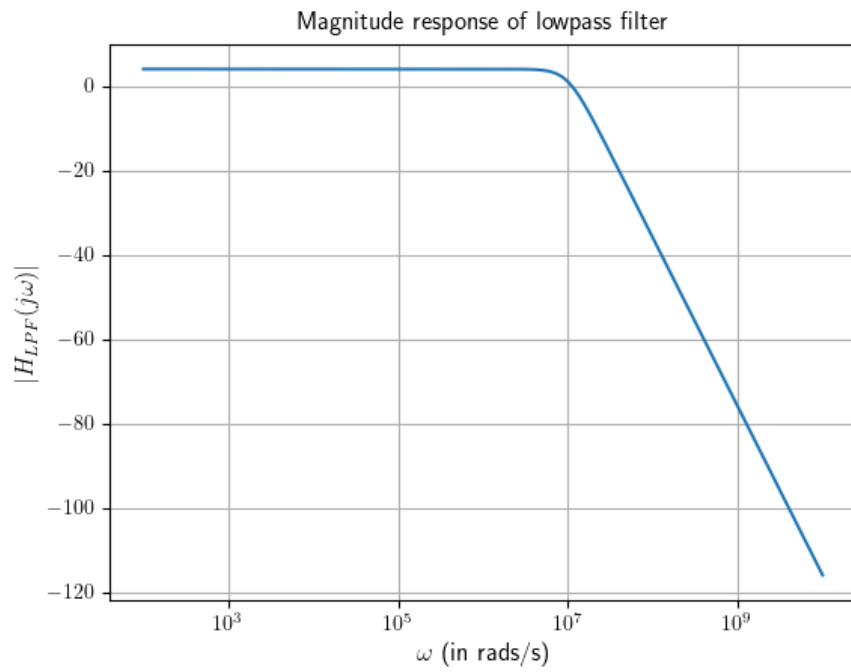


Figure 2: Magnitude response of lowpass filter

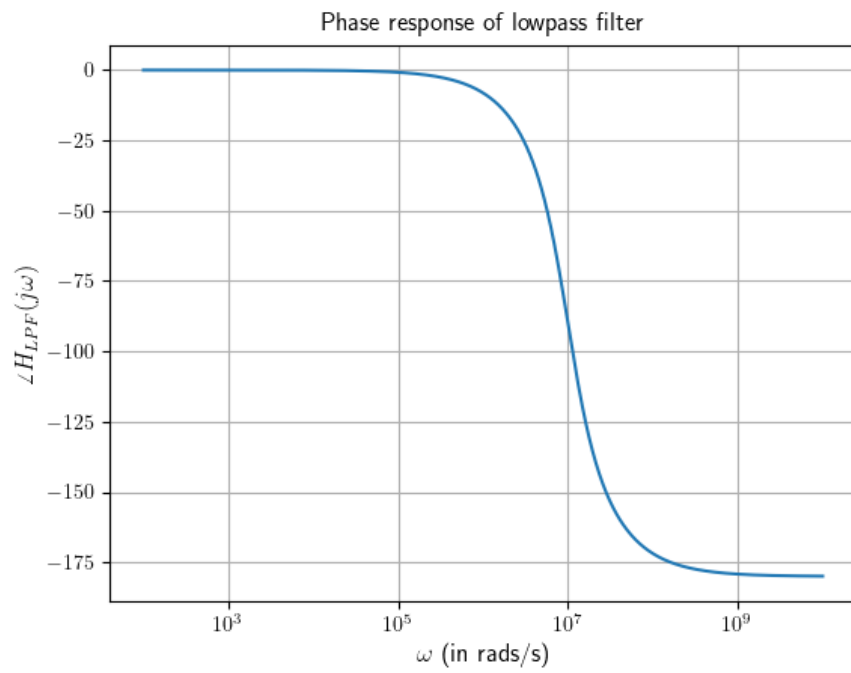


Figure 3: Phase response of lowpass filter

```
def freq_resp_lpf():
    s = sym.symbols('s')
```

```

A, b, V = lowpass(10000, 10000, 1e-11, 1e-11, 1.586, 1)
Vo = V[3]
# print(Vo)
num, den = Vo.as_numer_denom()
num, den = np.array(sym.Poly(num, s).all_coeffs(), dtype=float), np.
→ array(sym.Poly(den, s).all_coeffs(), dtype=float)
# num, den = [1.586], [1e-10, 1.414e-5, 1]
H = sp.lti(num, den)

global fignum

plt.figure(fignum)
fignum += 1
w = np.logspace(2, 10, 801)
w, mag, phi = H.bode(w)
plt.semilogx(w, mag)
plt.grid(True)
plt.title(r'Magnitude response of lowpass filter')
plt.xlabel(r'$\omega$ (in rads/s)', size=12)
plt.ylabel(r'$|H_{LPF}(j\omega)|$', size=12)

plt.figure(fignum)
fignum += 1
plt.semilogx(w, phi)
plt.grid(True)
plt.title(r'Phase response of lowpass filter')
plt.xlabel(r'$\omega$ (in rads/s)', size=12)
plt.ylabel(r'$\angle H_{LPF}(j\omega)$', size=12)

```

To get the step response  $s(t)$ , simply giving  $V_i(s) = 1/s$  and using impulse to get the time domain output voltage  $v_o(t)$ .

```

def q1():
    s = sym.symbols('s')
    A, b, V = lowpass(10000, 10000, 1e-11, 1e-11, 1.586, 1/s)
    Vo = V[3]
    num, den = Vo.as_numer_denom()
    num, den = np.array(sym.Poly(num, s).all_coeffs(), dtype=float), np.
→ array(sym.Poly(den, s).all_coeffs(), dtype=float)
    H = sp.lti(num, den)

    t = np.arange(0, 1e-5, 1e-8)
    t, y = sp.impulse(H, None, t)
    global fignum
    plt.figure(fignum)
    fignum += 1
    plt.plot(t, y)

```

```
plt.title(r'Step response ( $s(t)$ ) of lowpass filter')
plt.xlabel(r"time  $t$  (in seconds)", size=12)
plt.ylabel(r' $s(t)$ ', size=12)
plt.grid(True)
```

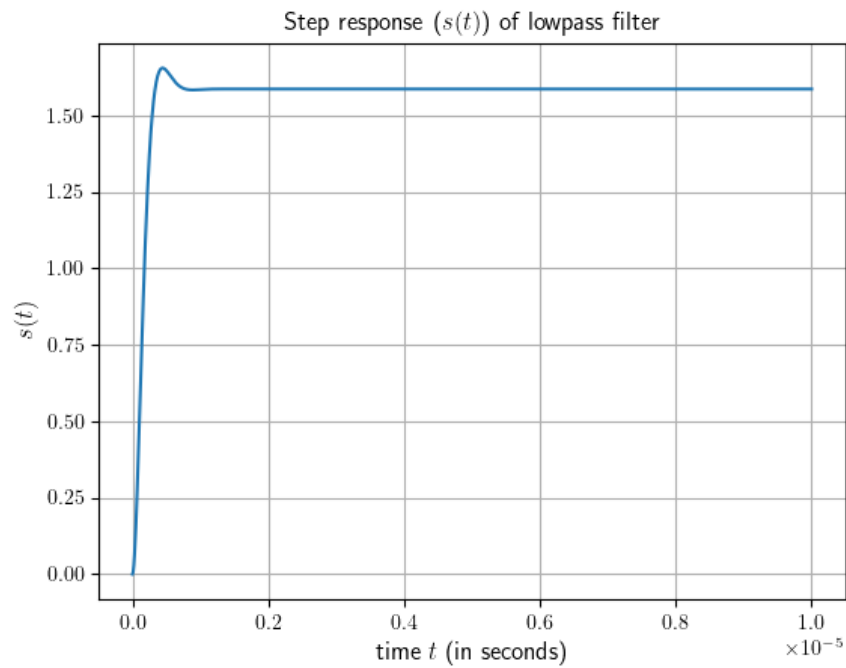


Figure 4: Step response of lowpass filter

### 3 High pass filter

The following circuit is considered.

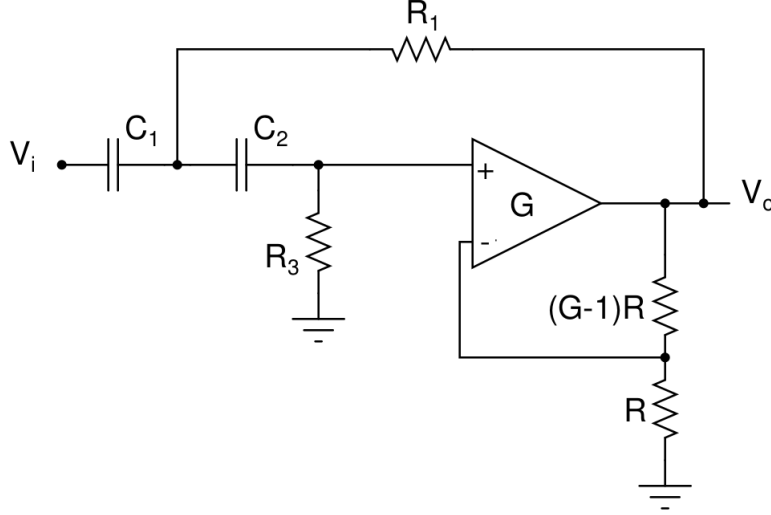


Figure 5: Circuit diagram of high pass filter

where, the Op-Amp is ideal and  $G = 1.586$ ,  $R_1 = R_3 = 10k\Omega$  and  $C_1 = C_2 = 1nF$ . This gives a second order Butter-worth filter with cutoff frequency of  $1/20\pi\text{MHz}$ .

As the op-amp is considered ideal, the circuit equations are

$$V_m = \frac{V_o}{G} \quad (5)$$

$$V_p = V_1 \frac{sC_2 R_3}{1 + sC_2 R_3} \quad (6)$$

$$V_p = V_m \quad (7)$$

$$(V_i - V_1)sC_1 + (V_p - V_1)sC_2 + \frac{V_o - V_i}{R_1} = 0 \quad (8)$$

These equations upon solving give the  $V_i$  to  $V_o$  transfer function as

$$\frac{V_o}{V_i} = 1.586 \frac{\frac{s}{10^{10}}}{1 + \frac{1.414s}{10^5} + \frac{s^2}{10^{10}}}$$

A similar function for highpass filter is also defined.

```
def highpass(R1, R3, C1, C2, G, Vi):
    s = sym.symbols('s')
    A = sym.Matrix([[0,0,1,-1/G],[(s*C2*R3)/(1 + s*C2*R3)
    → , -1,0,0],[0,1,-1,0],[1/R1+s*C1+s*C2,-s*C2, 0, -1/R1]])
    b = sym.Matrix([0,0,0,Vi*s*C1])
    V = A.inv()*b
    return (A, b, V)
```

When the following input voltage is given at  $V_i$

$$v_i(t) = (\sin(2000\pi t) + \cos(2 \times 10^6 t))u(t)$$

The transfer function is extracted using sympy and `lsim` is used to get the output voltage  $v_o(t)$ . This is done as shown below.

```

def q2():
    s = sym.symbols('s')
    A, b, V = highpass(10000, 10000, 1e-9, 1e-9, 1.586, 1)
    Vo = V[3]
    # print(Vo)
    num, den = Vo.as_numer_denom()
    num, den = np.array(sym.Poly(num, s).all_coeffs(), dtype=float), np.
    → array(sym.Poly(den, s).all_coeffs(), dtype=float)
    H = sp.lti(num, den)

    t = np.arange(0, 10e-3, 1e-7)
    vi = np.sin(2*np.pi*1e3*t) + np.cos(2*np.pi*1e6*t)
    t, vo = sp.lsim(H, vi, t)[:2]

```

The plots  $v_i(t)$  and  $v_o(t)$  for  $t < 10\mu s$  and  $t < 1ms$  are given below.

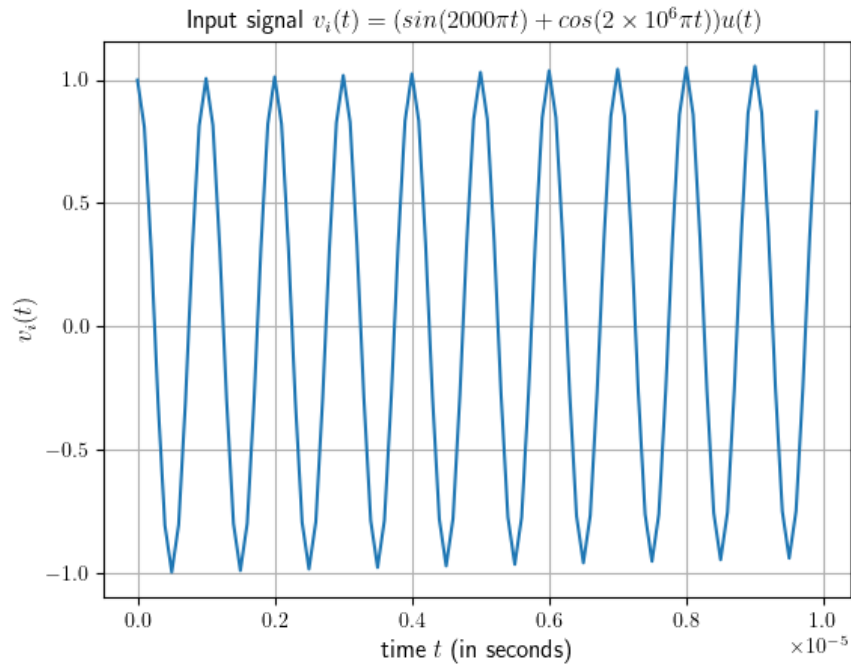


Figure 6: Input voltage for  $t < 10\mu s$

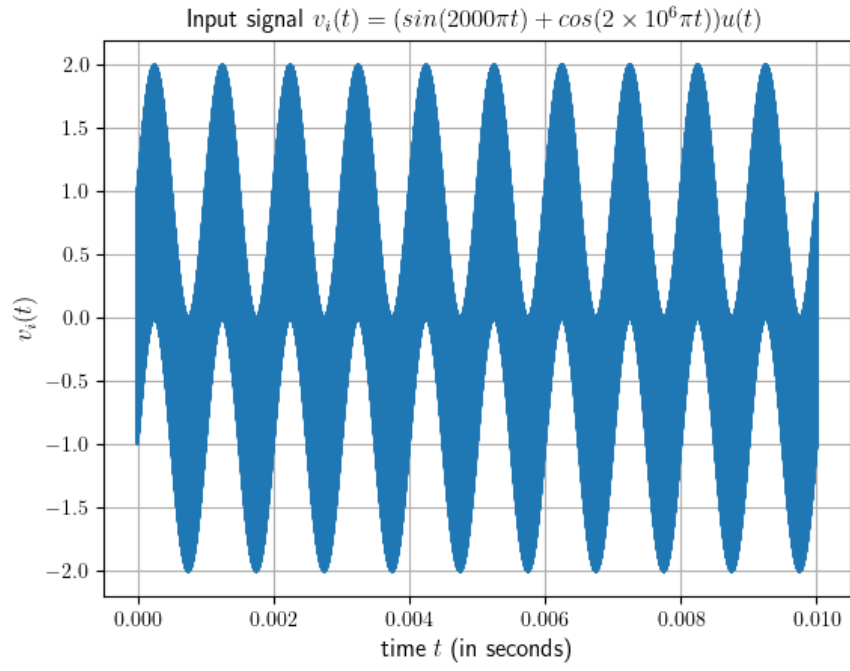


Figure 7: Input voltage for  $t < 1ms$

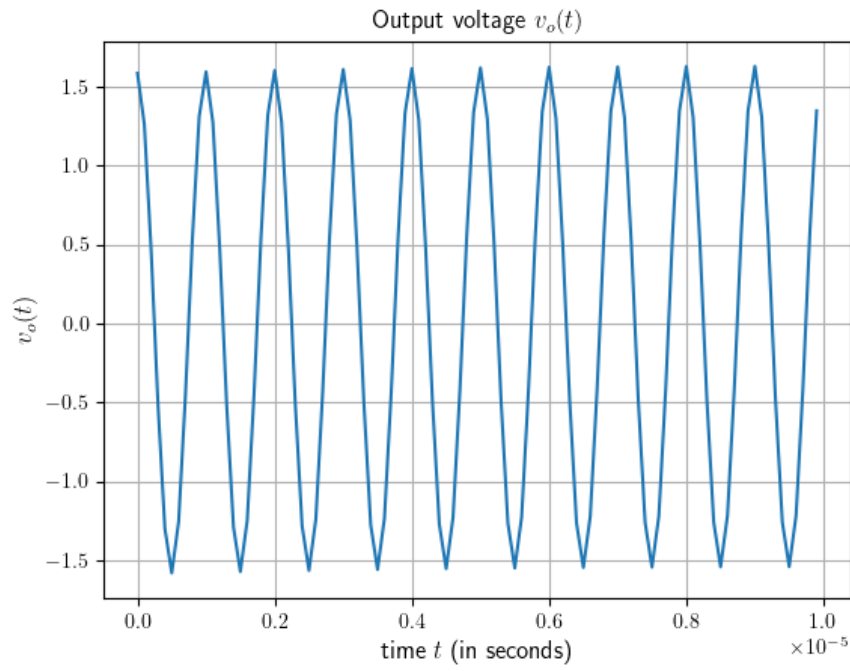


Figure 8: Output voltage for  $t < 10\mu s$



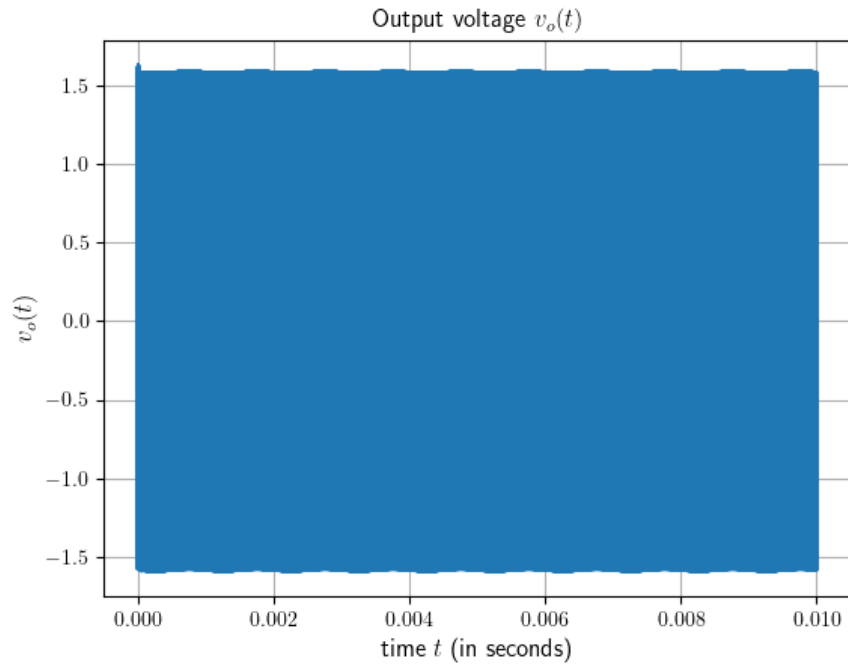


Figure 9: Output voltage for  $t < 1ms$

It can be seen clearly that the lower frequency  $\omega = 2000\pi$  component of  $v_i$  is attenuated and the higher frequency  $\omega = 2\pi \times 10^6$  component is amplified by 1.586 times.

The coefficients of the transfer function obtained using sympy are used to create the system transfer function using `lti` from `scipy.signal`.

From this, the frequency response of the system can be obtained. The plots of the frequency response are shown below.

```
def q3():
    s = sym.symbols('s')
    A, b, V = highpass(10000, 10000, 1e-9, 1e-9, 1.586, 1)
    Vo = V[3]
    # print(Vo)
    num, den = Vo.as_numer_denom()
    num, den = np.array(sym.Poly(num, s).all_coeffs(), dtype=float), np.
    → array(sym.Poly(den, s).all_coeffs(), dtype=float)
    H = sp.lti(num, den)

    w = np.logspace(0, 8, 801)
    w, mag, phi = H.bode(w)
```

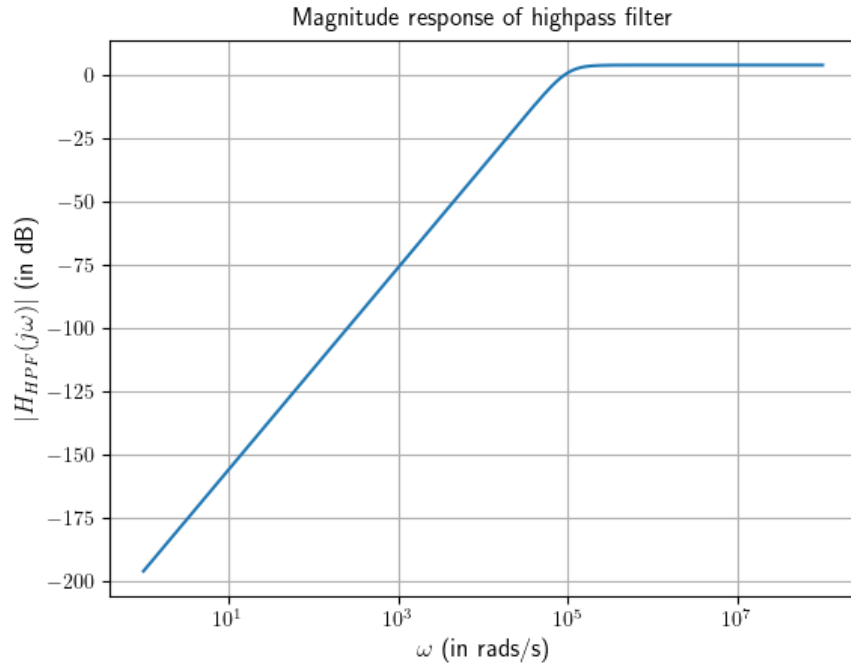


Figure 10: Magnitude response of high pass filter

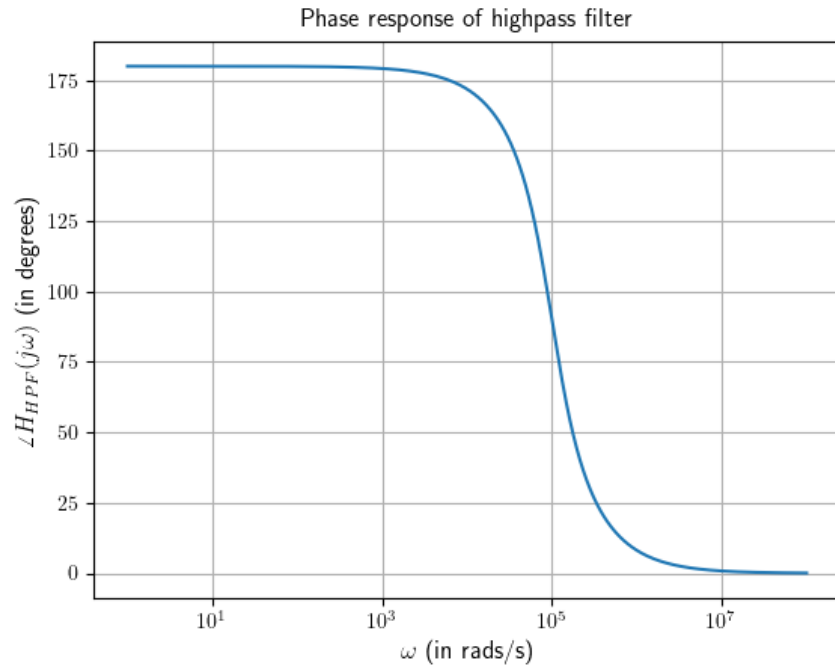


Figure 11: Phase response of high pass filter

Consider the input voltage  $v_i(t) = \exp(-10^4 t) \cos(10^7 t)$ , then it's laplace transform

$V_i(s)$  is given as

$$V_i(s) = \frac{s + 10^4}{(s + 10^4)^2 + 10^{14}}$$

This is given as input to the function `highpass` and the laplace transform of output voltage  $v_o(t)$  is obtained. `impulse` command is used to obtain the time domain signal.

```
def q4():
    s = sym.symbols('s')
    a, w0 = 1e4, 1e7
    Vi = (s+a)/((s+a)**2 + w0**2)
    A, b, V = highpass(10000, 10000, 1e-9, 1e-9, 1.586, Vi)
    Vo = V[3]
    # print(Vo)
    Vi_TF = sp.lti([1, a], [1, 2*a, w0**2 + a**2])
    num, den = Vo.as_numer_denom()
    num, den = np.array(sym.Poly(num, s).all_coeffs(), dtype=float), np.
    → array(sym.Poly(den, s).all_coeffs(), dtype=float)
    H = sp.lti(num, den)

    t = np.arange(0, 1e-4, 1e-8)
    vi = np.exp(-a*t)*np.cos(w0*t)
    t, h = sp.impulse(H, None, t)
```

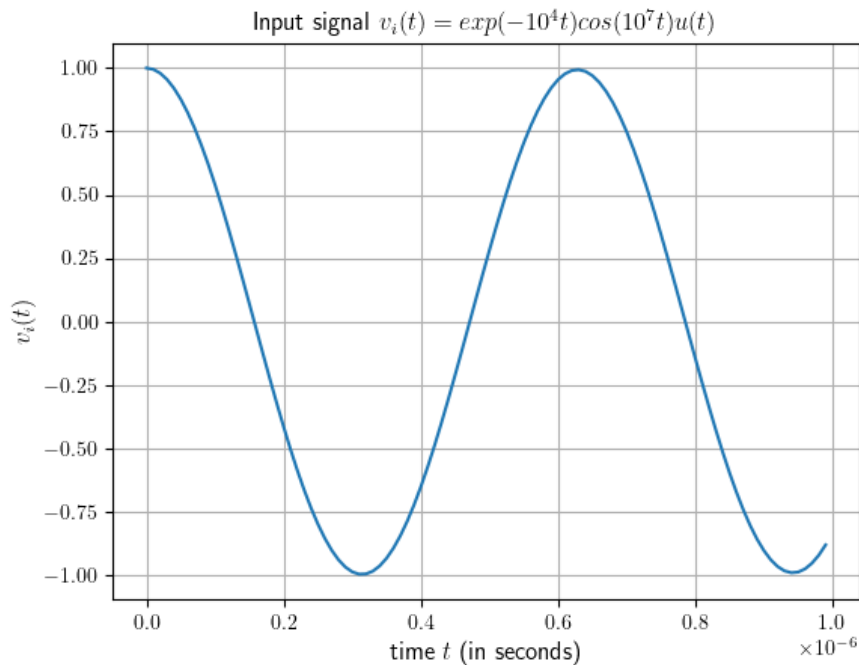


Figure 12: Input volatge for  $t < 1\mu s$

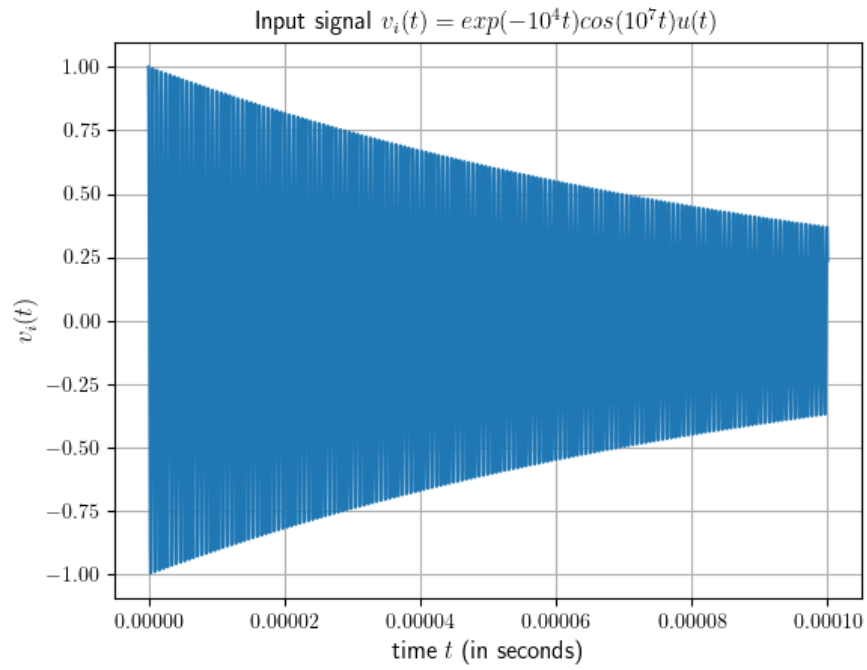


Figure 13: Input volatge for  $t < 100\mu s$

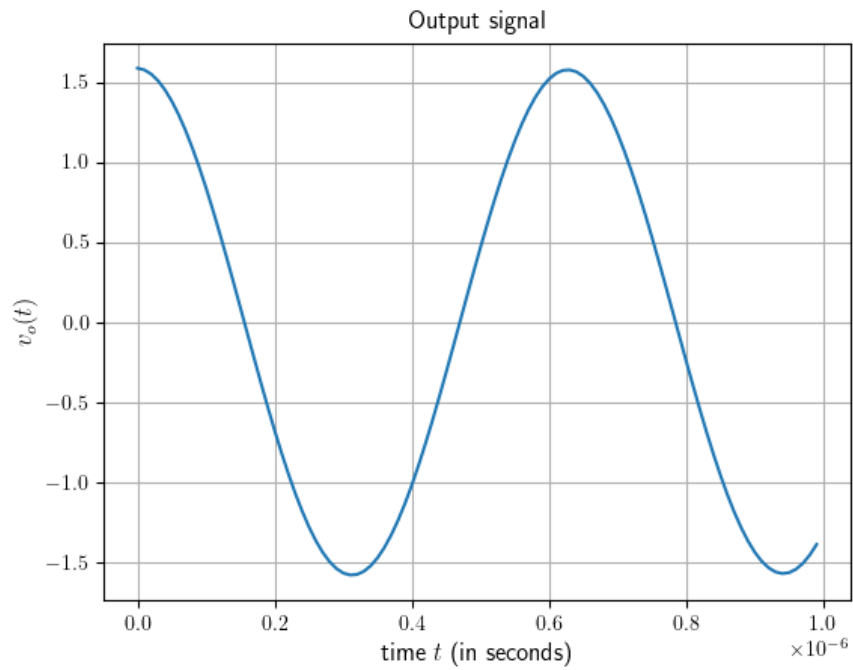


Figure 14: Output volatge for  $t < 1\mu s$

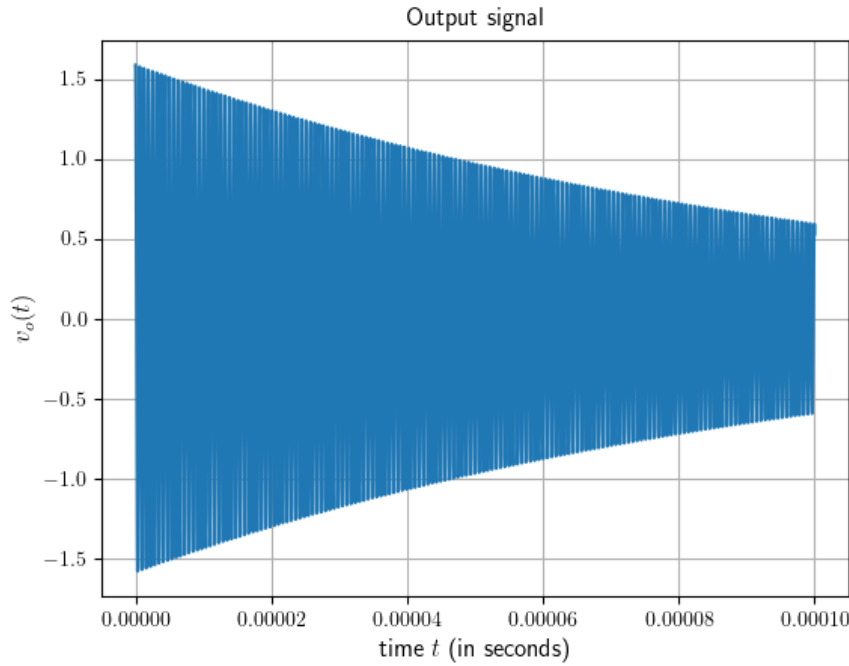


Figure 15: Output volatge for  $t < 100\mu s$

It can be seen that the signal is amplified by 1.586 times.

When the input voltage given is  $v_i(t) = \exp(-10t)\cos(10^3t)$ , then the laplace transform  $V_i(s)$  is given by

$$V_i(s) = \frac{s + 10}{(s + 10)^2 + 10^6}$$

The output voltage signal is obtained similarly.

```
def q4():
    s = sym.symbols('s')
    a, w0 = 1e1, 1e3
    Vi = (s+a)/((s+a)**2 + w0**2)
    A, b, V = highpass(10000, 10000, 1e-9, 1e-9, 1.586, Vi)
    Vo = V[3]
    # print(Vo)
    Vi_TF = sp.lti([1, a], [1, 2*a, w0**2 + a**2])
    num, den = Vo.as_numer_denom()
    num, den = np.array(sym.Poly(num, s).all_coeffs(), dtype=float), np.
    → array(sym.Poly(den, s).all_coeffs(), dtype=float)
    H = sp.lti(num, den)

    t = np.arange(0, 1, 1e-4)
    vi = np.exp(-a*t)*np.cos(w0*t)
    t, h = sp.impulse(H, None, t)
```

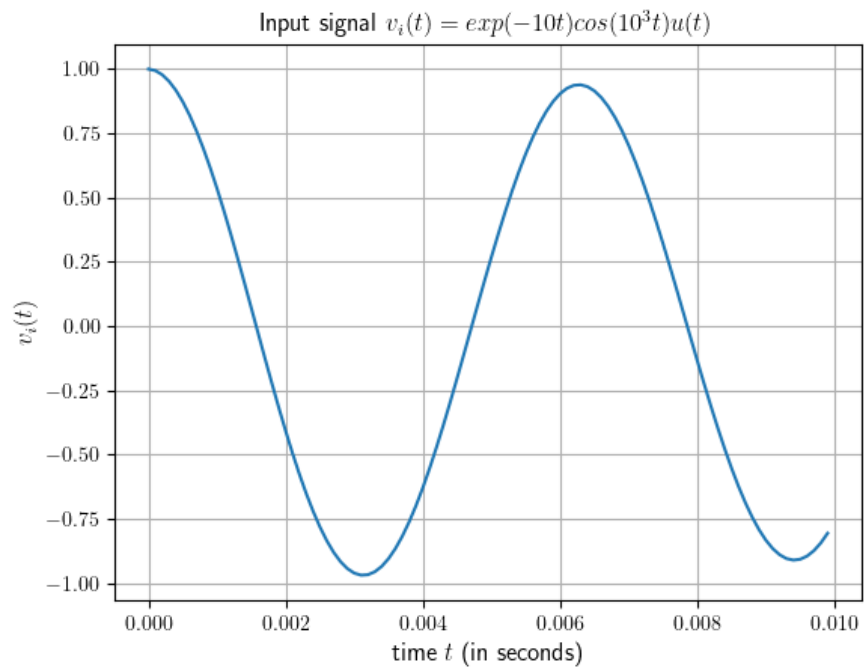


Figure 16: Input volatge for  $t < 10ms$

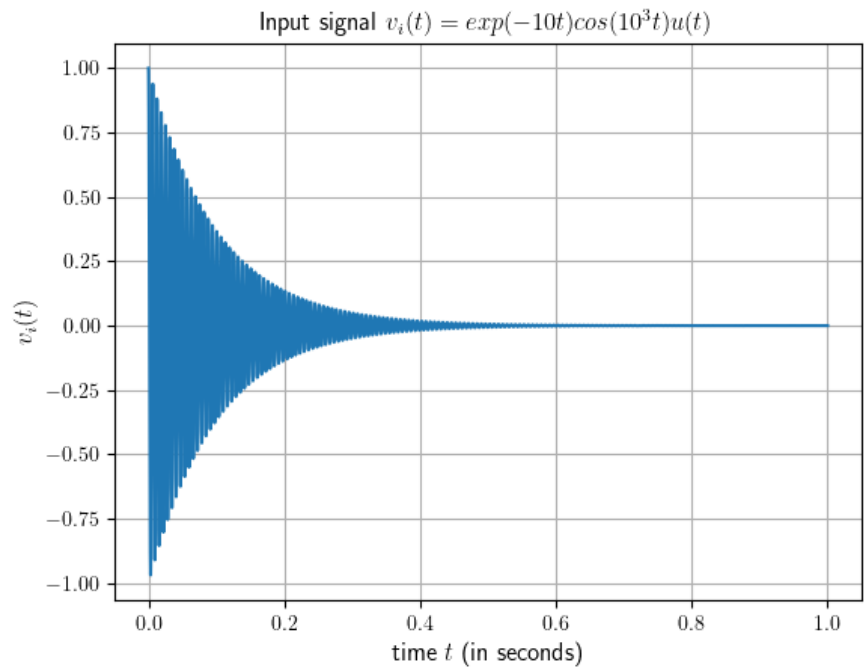


Figure 17: Input volatge for  $t < 1s$

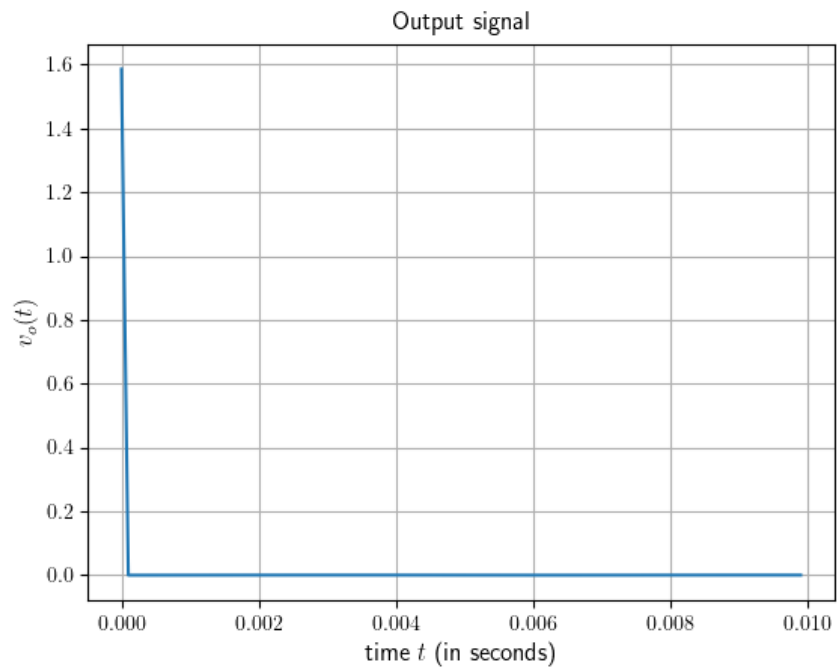


Figure 18: Output volatge for  $t < 10ms$

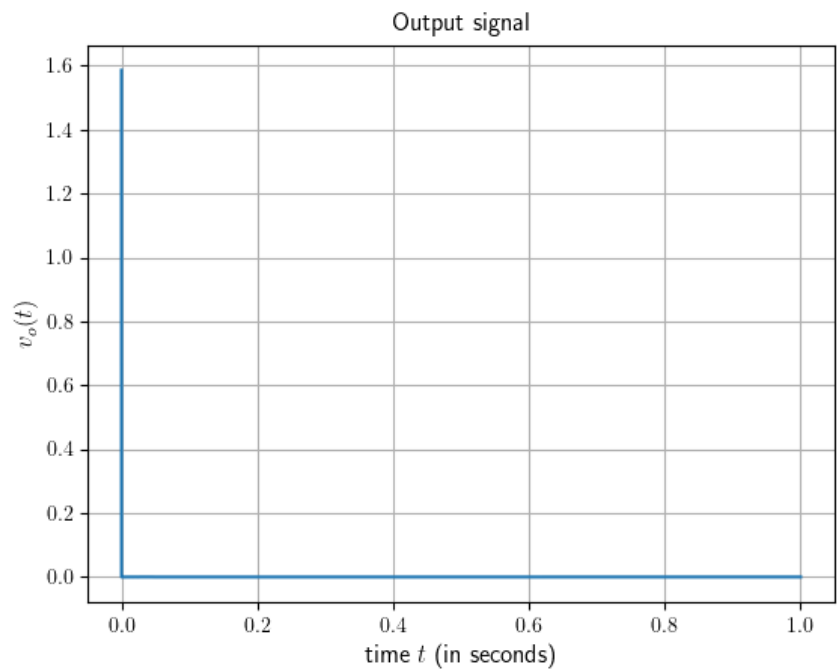


Figure 19: Output volatge for  $t < 1s$

It can be seen that the signal is attenuated.

Similarly, to get the step response, the laplace transform of input is given as  $V_i(s) = 1/s$  to the function `highpass` to get the laplace transform of output voltage signal.

```
def q5():
    s = sym.symbols('s')
    A, b, V = highpass(10000, 10000, 1e-9, 1e-9, 1.586, 1/s)
    Vo = V[3]
    # print(Vi)
    # Vi_TF = sp.lti([1, 0.01],[1, 2e-2, 1e7])
    num, den = Vo.as_numer_denom()
    num, den = np.array(sym.Poly(num, s).all_coeffs(), dtype=float), np.
    → array(sym.Poly(den, s).all_coeffs(), dtype=float)
    H = sp.lti(num, den)

    t = np.arange(0, 1e-3, 1e-7)
    t, h = sp.impulse(H, None, t)
```

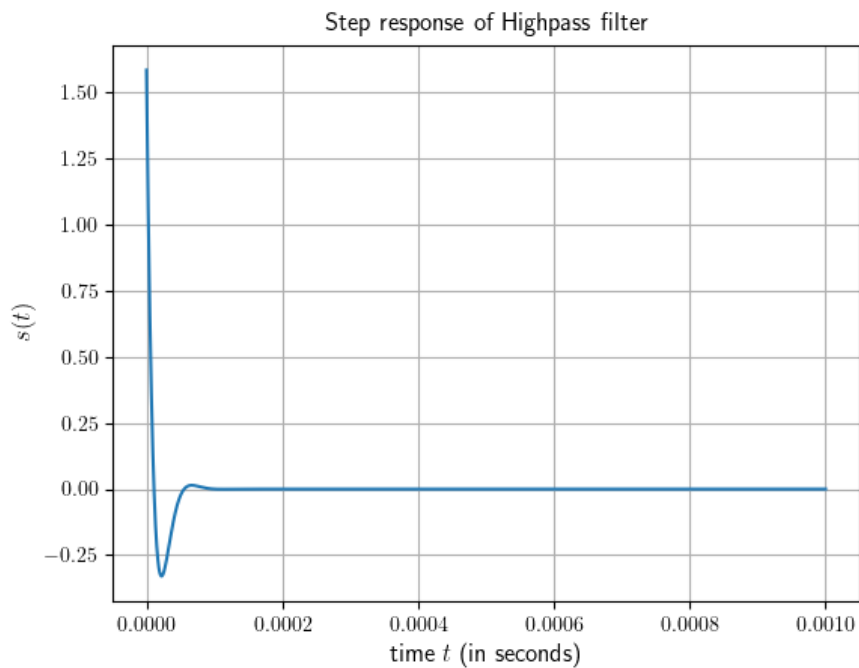


Figure 20: Step response of high pass filter